

Index

A

absolute jitter 14
amplitude modulation 17
AM-to-FM noise conversion 186

B

Barkhausen criterion 5

C

Colpitts oscillator 67, 89
 current source noise 78
 differential 91
 noise sources 72
 resistor noise 74
 transistor noise 78
complementary differential oscillator 94
current source noise in Colpitts oscillator 78
current-biased differential oscillator 85, 96
cycle-to-cycle jitter 16

D

Demir's model 28
design example
 oscillator for GSM receiver 99, 129
device stress, effect on amplitude 122
differential oscillator 35, 94
 current biased 85, 96
 differential pair noise 50
 resonator noise 44
 tail current noise 57
 voltage biased 88
diffusivity 15

E

example
 oscillator for GSM receiver 99, 129

F

figure of merit 83, 132

FLEX oscillator 168
flicker noise 96, 110, 166
 jitter 15
 Leeson's model 8
 nulling 168, 172
 top-biased oscillator 113
FM noise
 AM-to-FM conversion 186
 current source 155
 due to switch 151
 Groszkowski 142

G

Groszkowski 142
GSM phase noise requirements 99

H

Hajimiri's model 25
harmonic balance 84

I

impulse sensitivity function (ISF) 25

J

jitter 12
 flicker noise 15

K

Kartner 29

L

\mathcal{L} (noise-to-carrier ratio) 8, 19
Leeson's formula ix, 8, 38, 62, 97
linear oscillator 3
linewidth 15, 21
Lorentzian spectrum 23

M

modulation 17

N

noise factor
Colpitts oscillator 78
differential oscillator 104
FET (γ) 61
Leeson 38, 62, 97
noise filtering 112
earlier work 125
wideband 172
noise sensitivity curve 184

O

oscillator
Colpitts 67, 89
complementary differential 94
current-biased differential 85, 96
design example
GSM receiver 99, 129
differential 35
figure of merit 83, 132
ideal model 1
linear 3
noise filtering 112
van der Pol 142
voltage-biased differential 88

P

period jitter 16
phase jitter 15
phase modulation 17
phase noise 19, 104
Colpitts 72
flicker noise 139, 166
FM due to current source 155
FM due to Groszkowski 142
FM due to switch 151
thermal 39
power supply rejection 119

R

resistor noise 6
in Colpitts oscillator 74
resonator noise in differential oscillator 44

S

single sideband 19
stress, effect on amplitude 122
supply rejection 119
supply sensitivity 187

T

tail current noise in differential oscillator 57
transconductor noise 6
transistor noise in Colpitts oscillator 78
tuning range 123
tuning sensitivity 187

V

van der Pol oscillator 142
varactor 175
noise sensitivity 181
voltage-biased differential oscillator 88