

Contents

Chapter 1 Basics of LC Oscillators	1
1 Introduction.....	1
2 The Mathematical Oscillator	1
3 Additive White Noise in LC Oscillators	3
4 The Linear Oscillator	3
4.1 Warning	3
4.2 Linear System Theory Applied to Oscillators	4
5 Linear Oscillator Noise Analysis	6
6 How Is This Book Different?.....	8
Chapter 2 Oscillator Purity Fundamentals	11
1 Introduction.....	11
2 Timing Jitter.....	12
3 Recognizing Phase Noise.....	17
4 Single Sideband Contains AM and PM	19
5 Phase Noise.....	19
6 Oscillator Phase Noise Models: Post-Leeson	24
6.1 Hajimiri's Model.....	25
6.2 Demir's Model.....	28
6.3 A Mechanistic Physical Model for LC Oscillators	31
Chapter 3 Current Biased Oscillator	35
1 Steady-State Operation	35
2 Linear Analysis of Differential Oscillator	37
3 Thermally Induced Phase Noise	39
3.1 Resonator Noise.....	44
3.2 Differential Pair Noise	50
3.3 Tail Current Noise	57
3.4 Proving Leeson's Hypothesis	62
4 Validation of Thermal Noise Analysis	63
Chapter 4 Colpitts Oscillator	67
1 Introduction.....	67
2 Steady-State	67
3 Phase Noise Analysis.....	72
3.1 Noise Sources	72

3.2	Noise in the Resistor	74
3.3	Noise of the Current Source and the Transistor	78
3.4	Noise Factor of Colpitts Oscillator	78
4	Conclusions	80
Chapter 5 Design for Low Thermal Phase Noise		83
1	Introduction	83
1.1	Oscillator Figure of Merit	83
2	Note About Harmonic Balance in LC Oscillators	84
3	Amplitude in Differential LC Oscillators	85
3.1	Current-Biased Differential Oscillators	85
3.2	Voltage-Biased Oscillator	88
3.3	Colpitts Oscillators	89
3.4	Complementary Differential Oscillator	94
4	Design of Current-Biased Differential Oscillators	96
5	A Design Example	99
5.1	Design Requirements	99
6	Intuitive Explanation of Phase Noise Sources	104
7	Loading in Current-Biased Oscillators	106
8	Sizing of the Current Source Device	109
9	Noise Filtering in Oscillators	110
9.1	Role of the Current Source	110
9.2	Noise Filtering	112
10	Prototype Oscillator	116
11	Practical Considerations	119
11.1	Power Supply Rejection with Noise Filtering	119
11.2	Device Limitations on Maximum Swing	122
11.3	Extending the Tuning Range	123
11.4	Noise Filtering in Earlier Works	125
11.5	Noise Filtering in Other Oscillators	126
12	Example: Redesign of GSM VCO	129
13	Anatomy of the Figure-of-Merit	132
Chapter 6 Flicker Noise		139
1	Flicker Induced Phase Noise	139
2	FM Due to Modulated Frequency Content	139
2.1	Groszkowski in a van der Pol Oscillator	142
2.2	Groszkowski in the Differential Pair Oscillator	144
2.3	Critical Oscillation	146
2.4	Hard Limiting	149
3	Switch Voltage Noise Modulates Capacitance	151
4	Frequency Modulation by the Current Source	155
Chapter 7 Design for Low Flicker Phase Noise		165
1	Introduction	165
2	Flicker Noise Minimization	166

3	Nulling Flicker Noise.....	168
4	Wideband Nulling of Flicker Noise Up Conversion	172
Chapter 8 The Role of the Varactor		175
1	Fundamentals	175
2	Types of Varactors.....	179
3	Varactor Tuning.....	180
4	Analytical Evaluation of Noise Sensitivity.....	181
5	AM-to-FM Noise Conversion.....	186
6	Tuning and Supply Sensitivity.....	187
7	Measurements and Simulation Results	190
8	Discussion.....	194